

Arduino Bootcamp : Learning Through Projects

Stopwatch - Controlling a 4 Digit Segment Display - Part 1




Project Objectives

- In this project you will learn:
 - How to connect a 4 digit seven segment display in a circuit
 - Controlling the 4 digit segment display in code

Parts


- Arduino Uno
- USB A-B cable
- Breadboard
- 4 Digit Seven Segment Display (Common Anode)
- 7 × 220 ohm resistors
- Connecting wires

4 Digit Seven Segment Display

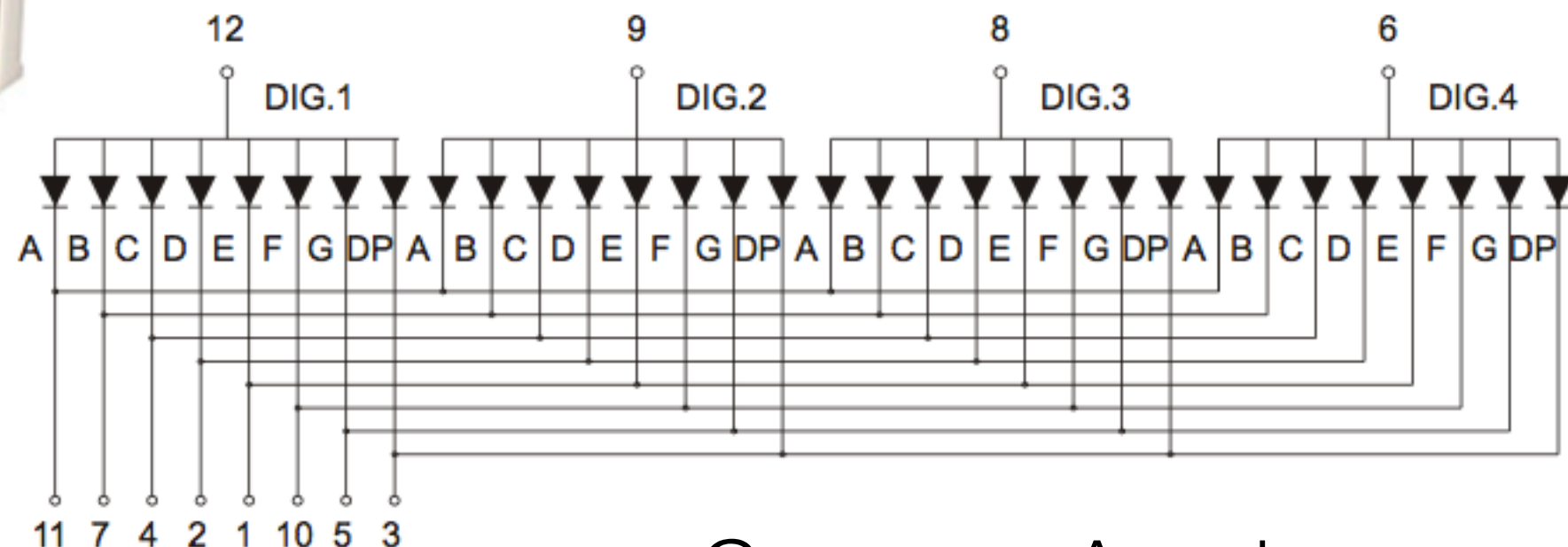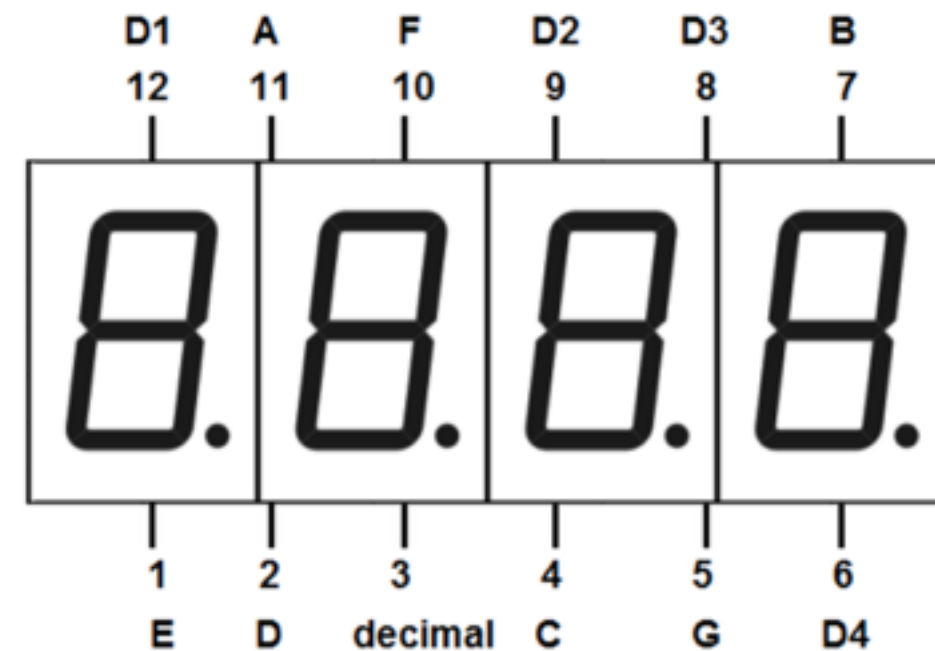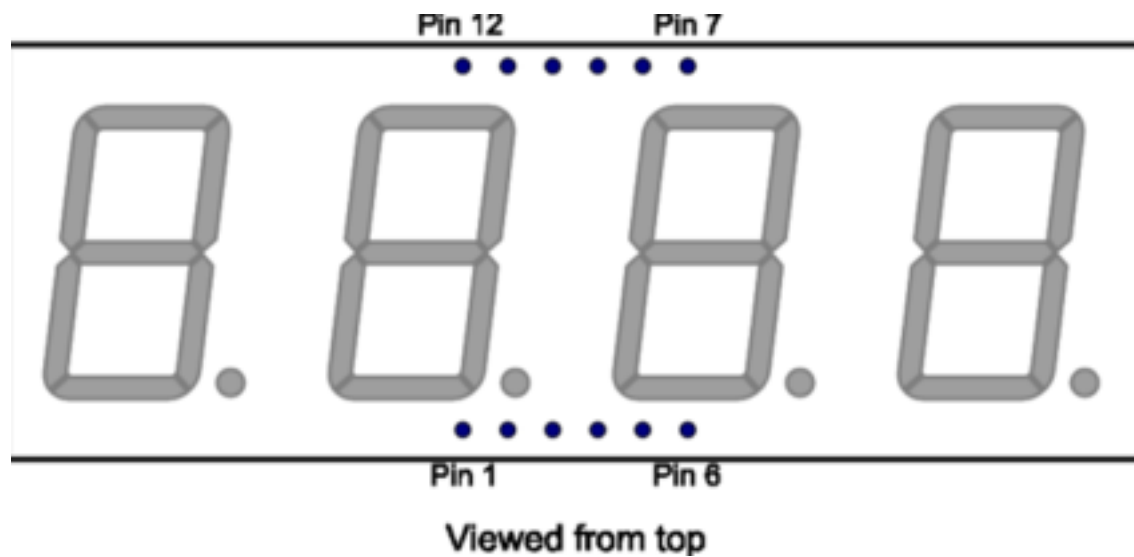

Common Anode

Circuit Diagram

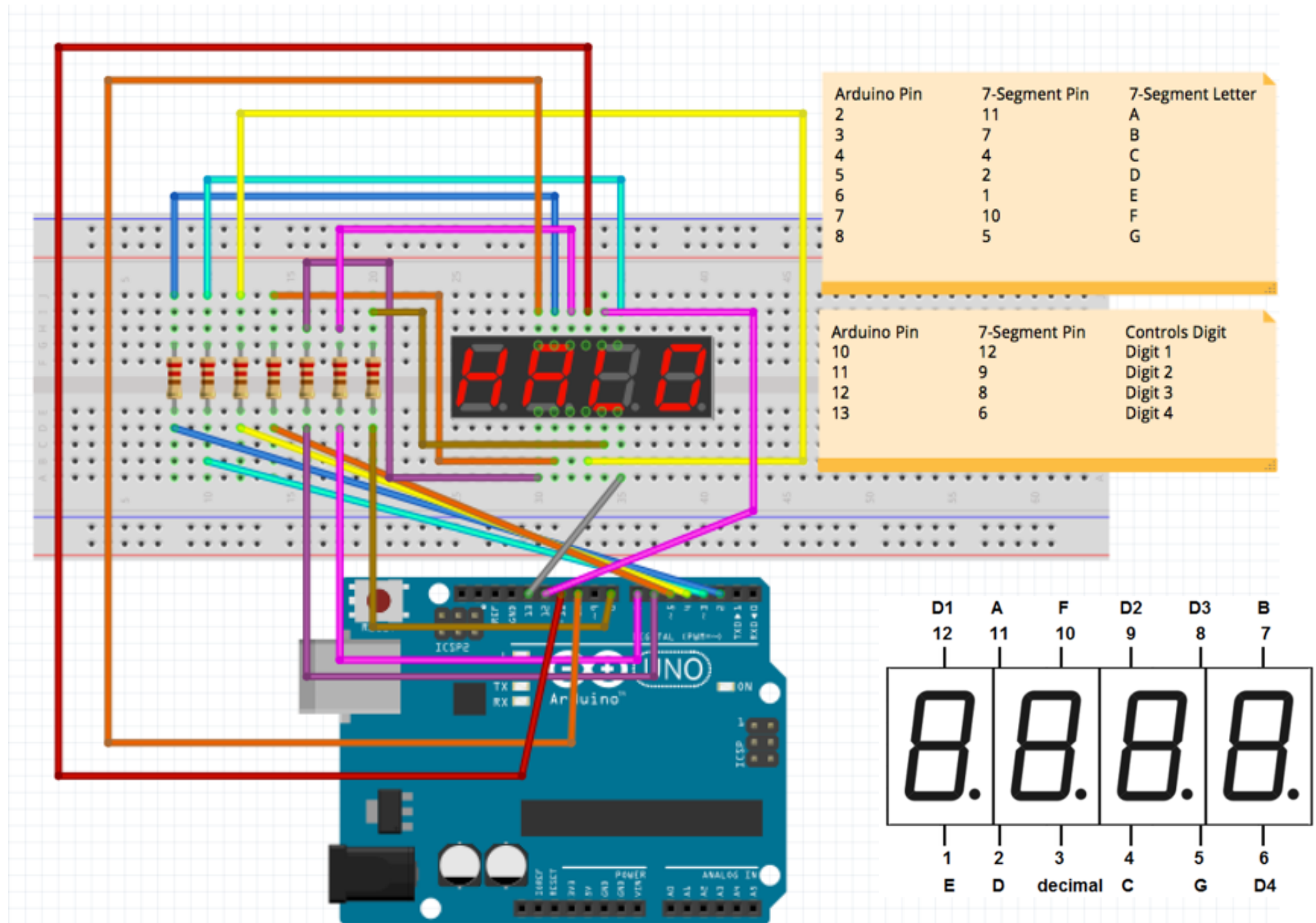

Summary

- In this project you learnt:
 - How to connect a 4 digit seven segment display
 - How to write to the display in code